

Part 1: Introduction to Data Acquisition (DAQ) - *Input*

How do you get
data *into*
(and out of)
a computer?



Data Acquisition (DAQ)



The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition



**What is the
temperature
outside?**

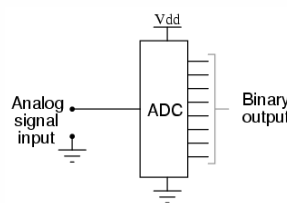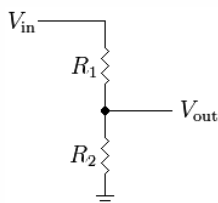*How do you get
that **value** into
a computer?*




Utility

Without DAQ, then we would all be theoretical neuroscientists.

Data Acquisition (DAQ)

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

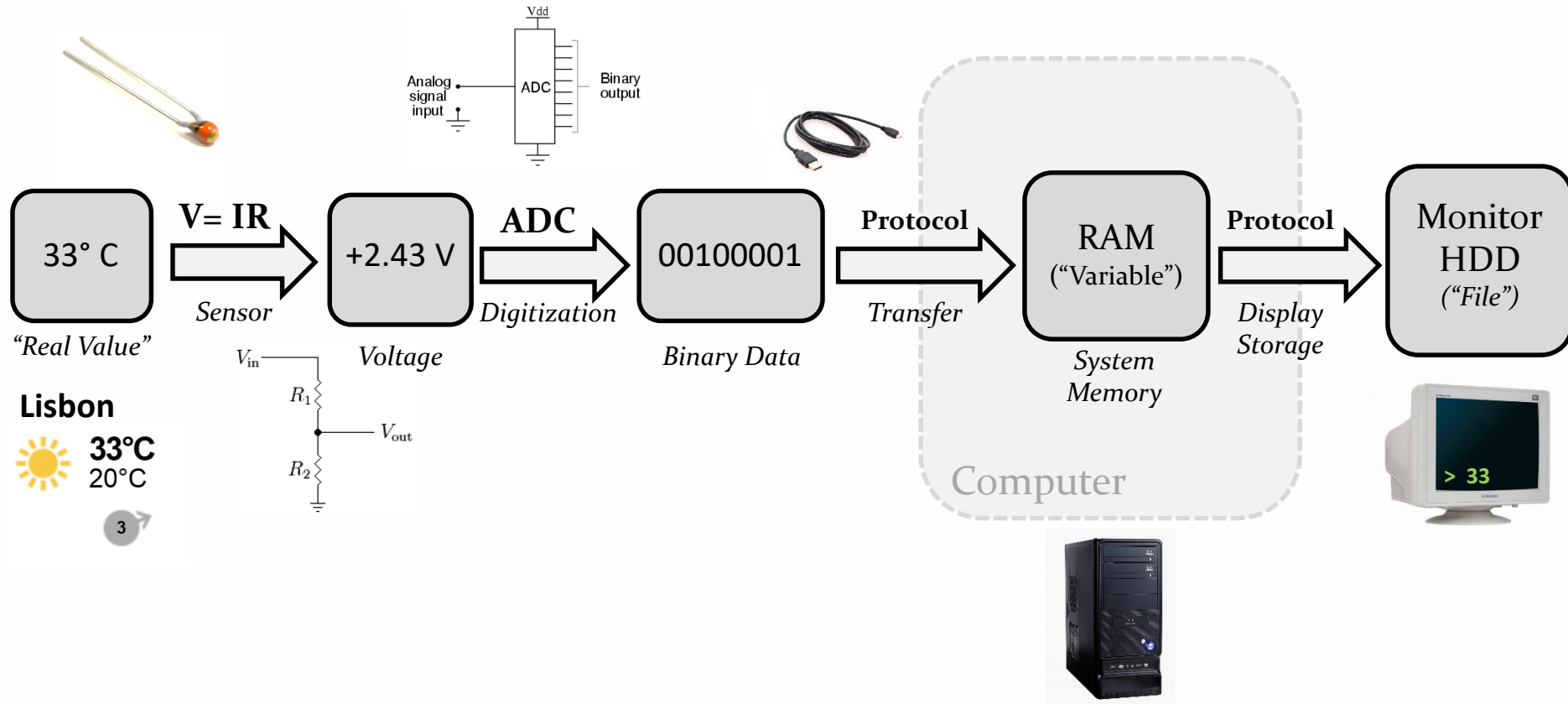

Utility



Anything is measurable...and everyone should know how to do this.



Sensor (voltage transducer)

Computers can only measure voltage. Therefore, any real-world quantity must be converted into a voltage before it can be measured and digitized.


Definition

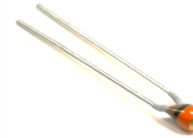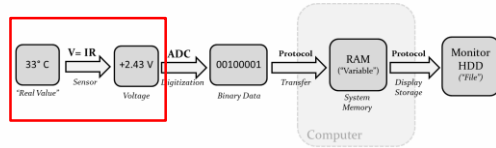

LDR, **Thermistor**, Photodiode, etc.

Camera, E-phys System

Microphone, Keyboard, Touchscreen

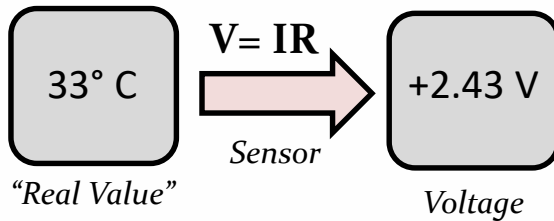


Utility



Ohm's Law


A linear relationship between Voltage, Current and Resistance exists for “Ohmic” circuit elements. This

Definition

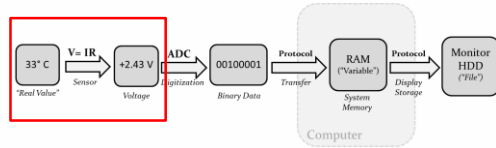

$$V = IR$$

Ohm's Law

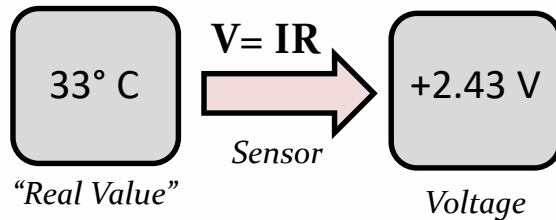

V - Voltage: Force pushing electrons
(Volts)

I - Current: Number of electrons/second
(Amps)

R - Resistance: Ease to electron flow
(Ohms)



Ohm

Utility




This linear relationship between passive circuit elements will solve the majority of electronics dilemmas.



Voltage Divider

Two resistors will proportionally attenuate a voltage as current flows from a source to ground. This relationship can be used to create an intermediate voltage dependent on a variable resistor.

Definition

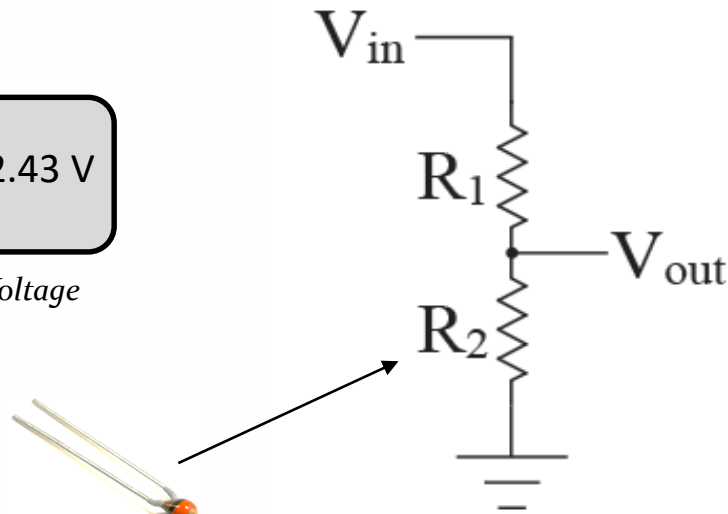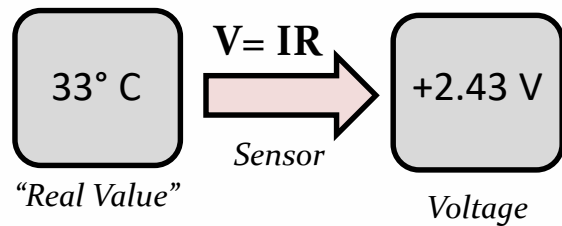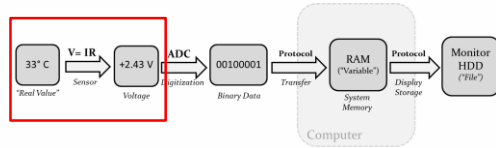

$$V_{out} = V_{in} * \frac{R2}{(R1 + R2)}$$


Voltage Divider

Utility




This circuit is everywhere in modern circuits. A sensor can be constructed by simply making one of the resistors dependent on a “real world” quantity. (pressure, temperature, light, rotation...sweat...anything!)

Analog to Digital Converter (ADC)

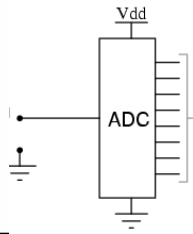An integrated circuit that converts analog values to binary (digital) representation. They come in many flavours, speeds and bit depths.



Definition

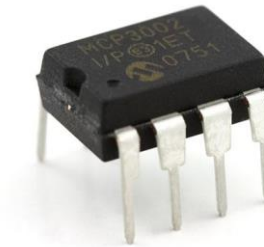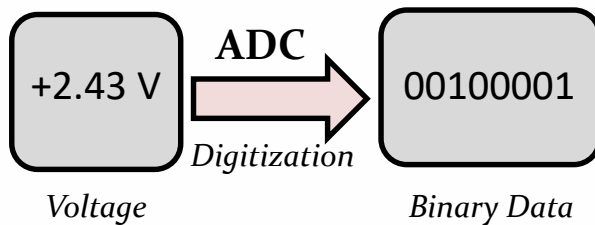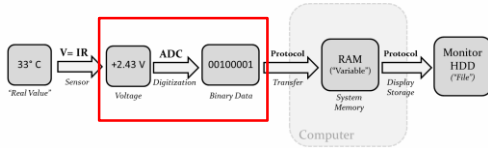

An ADC converts analog voltage to a binary representation.

(Relevant Characteristics)

- **How fast?** (Sample Rate, Hz)
- **Resolution?** (#bits per sample)
- **Range** (of input voltage)

Utility



ADCs are everywhere. In your digital cameras, smartphone, and GPS. Everything a computer knows about the “real-world” goes through an ADC. There are many types, with many different features (speeds, resolution, noise, channels...).




Digital Input

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

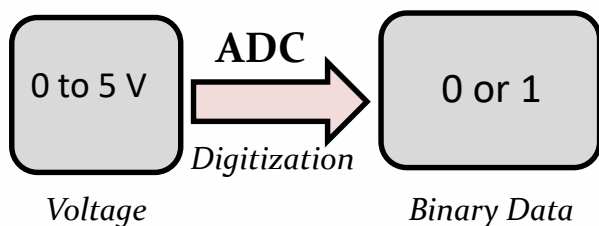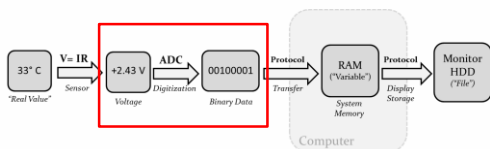

Voltage Comparator

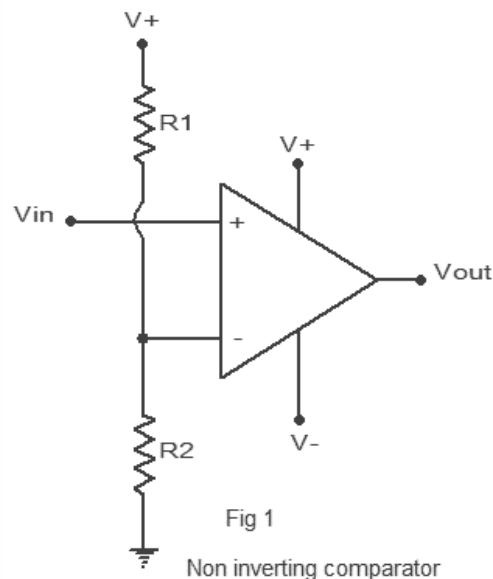

The simplest ADC: 1-bit


Utility

The “simplest” computer input. 0 or 1.



Analog Input: Flash ADC

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

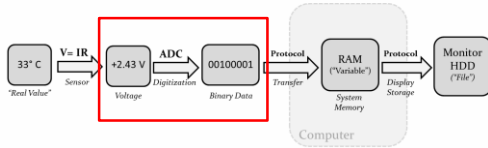

Serial Voltage Divider

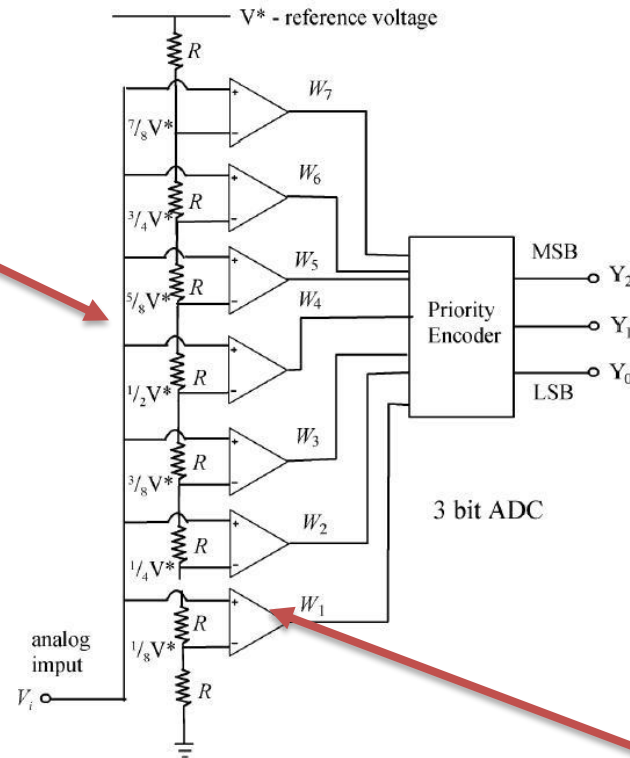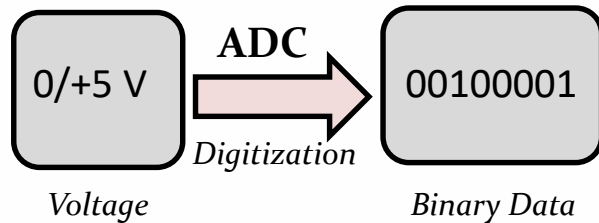

Fast
Low Bit Depth
Large!

Flash ADC

Comparator




Utility

An easy to understand, but not often used version of an ADC. Very, very fast...but low bit depth.

Analog Input: Successive Approximation ADC

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

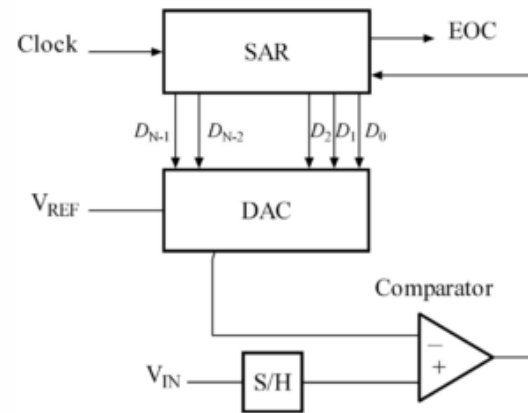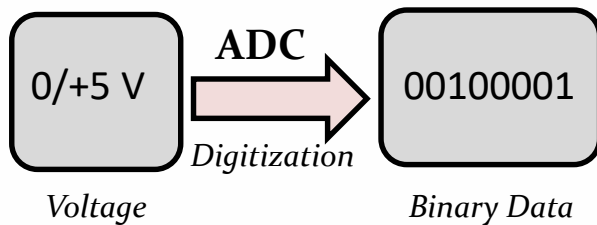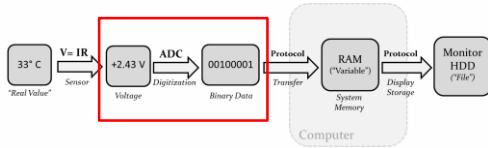

Slow(er)
High Bit Depth
Small

Successive Approximation ADC

Utility



Much more common form of ADC.



Communication Protocol

A standard procedure for transferring binary information between digital devices,

Definition

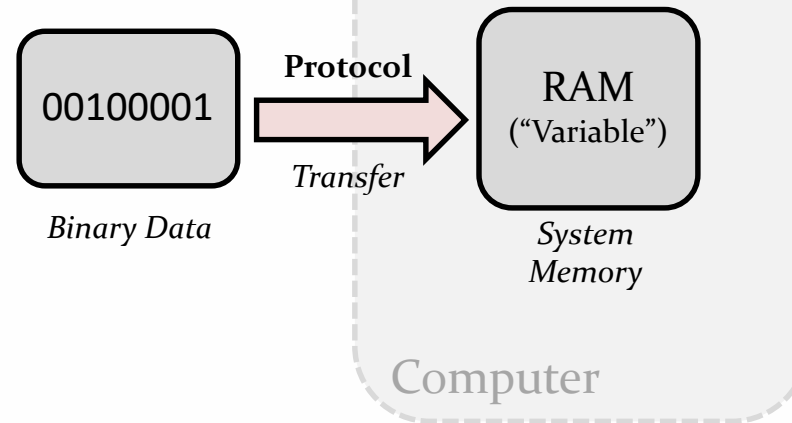
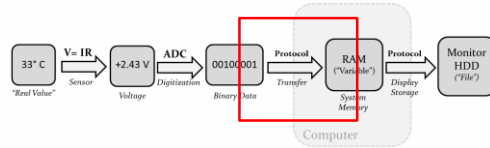


Utility

Serial Port (USART/USART – RS-232)

A standard procedure for transferring binary information between digital devices,

Definition

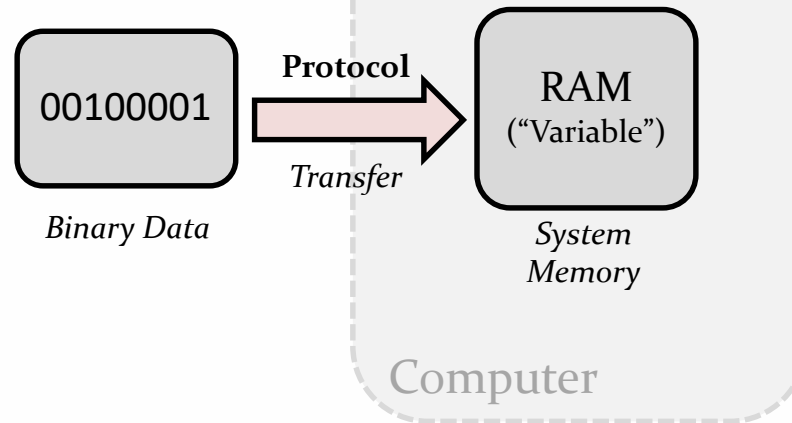
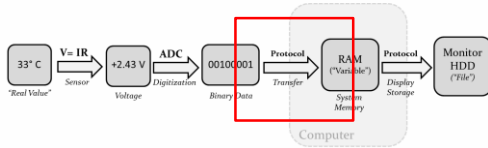


Utility

System Memory (RAM)

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

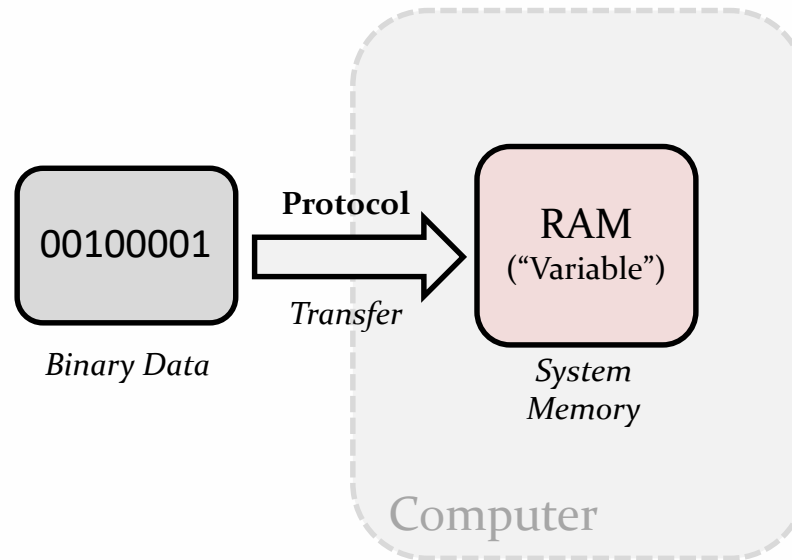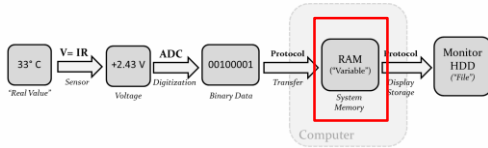

Utility


You can only “work” with data in System memory. This is where you can start doing analysis...oting data to other devices for control of storage. This is when your data is IN the computer.



Data Display/Storage

This is technically data “output”...but just for completeness.

Definition

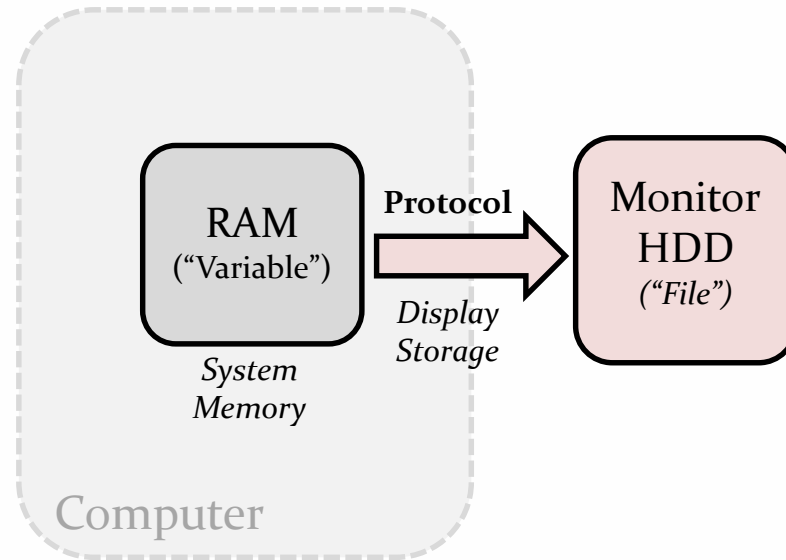


Utility



Data Acquisition (DAQ)

The process of measuring a real-world value via voltage conversion, digitization, and transfer to system memory. (for subsequent processing and storage).

Definition

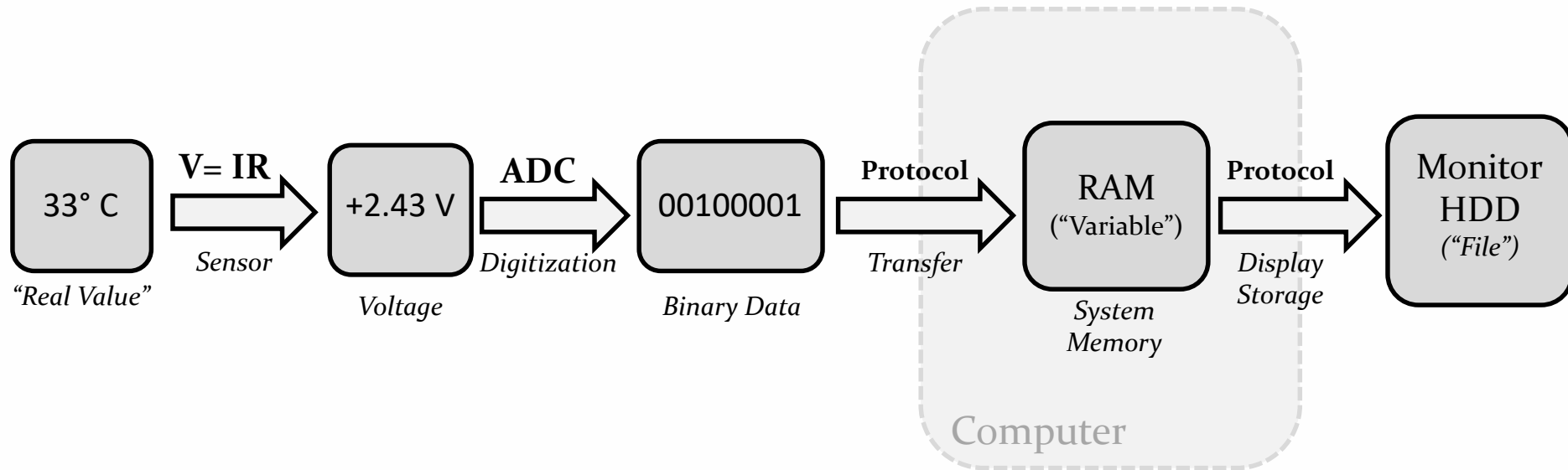

This is how computers know about the world.

Utility



Microcontroller Worksheet


DAQ and Control with a simple microcontroller.

Definition

We



Utility

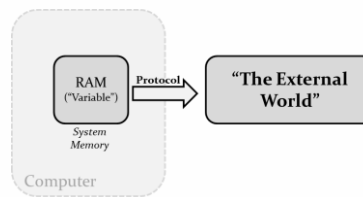

Part 2: Introduction to Actuation– Output


How do you get
data *into*
(and out of)
a computer?



Control (with a binary computer)

Conversely to acquisition, computers can only output voltages.

Definition

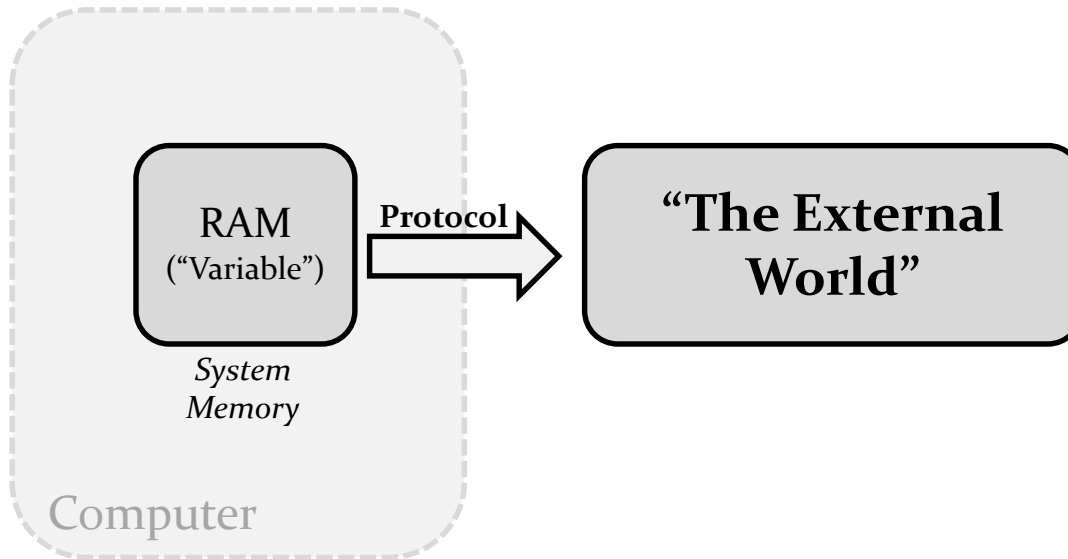

If you want to...

- "Play a tone"
- "Make something move"
- "Turn on a light"
- "Open a valve"
- "Show a movie"
- ... etc.


Utility



Control (with a binary computer)

Conversely to acquisition, computers can only output voltages.

Definition

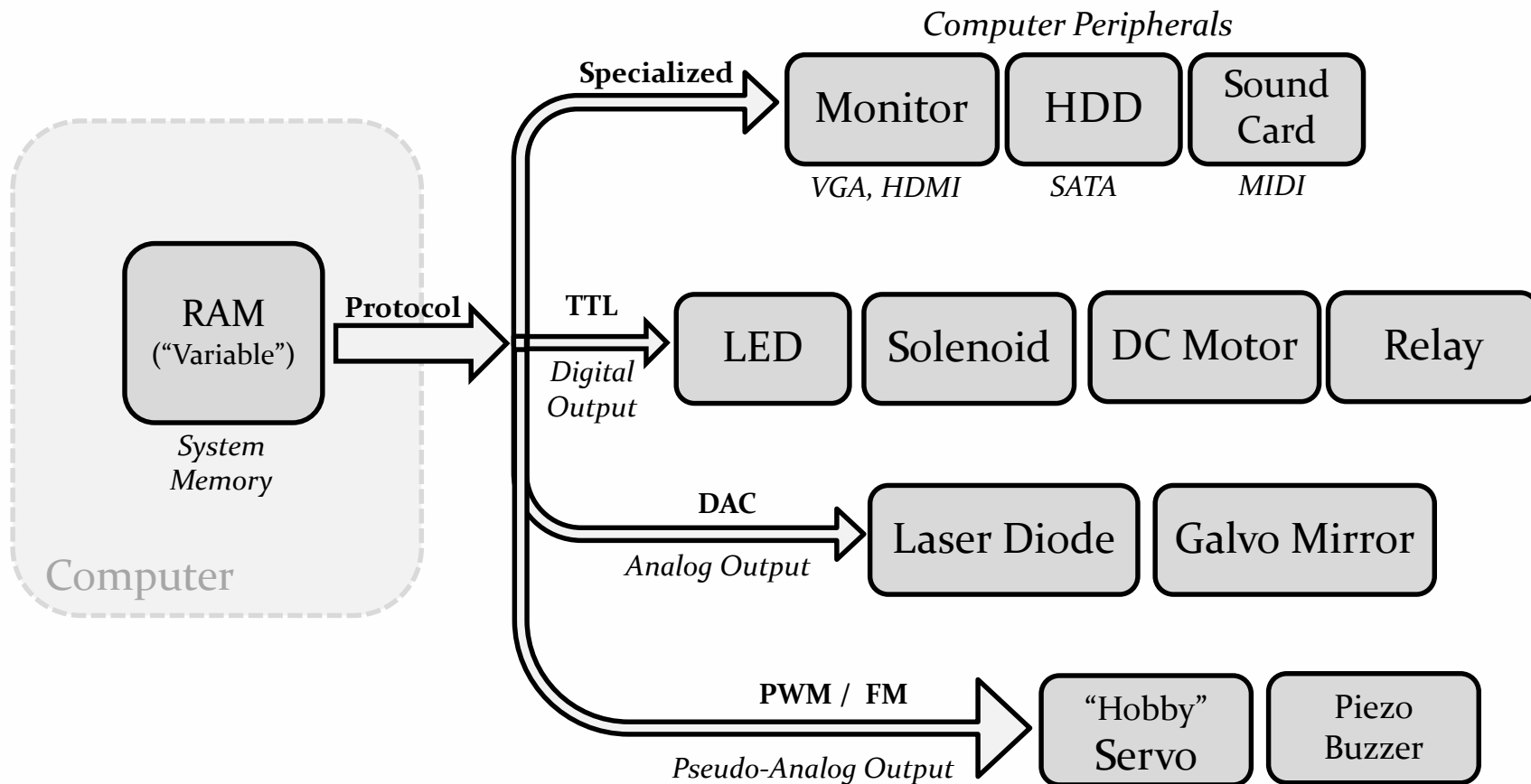


Utility



Digital Output

Conversely to acquisition, computers can only output voltages.

Definition

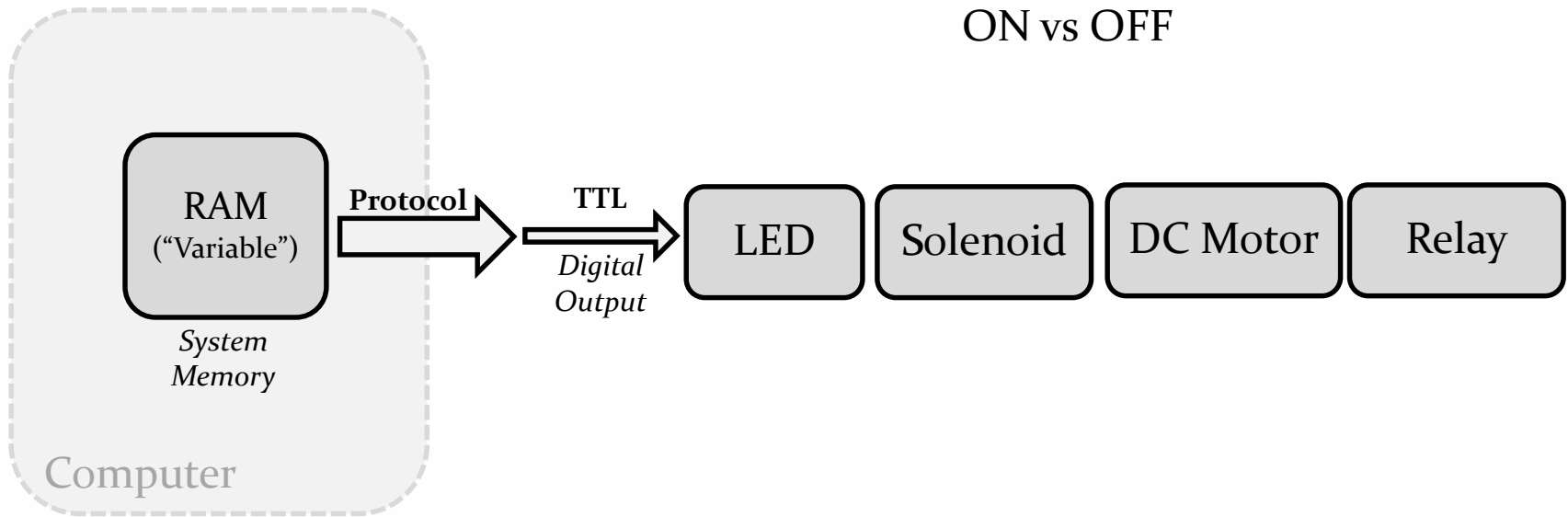

Utility





TTL: Transistor-Transistor Logic

Conversely to acquisition, computers can only output voltages.

Definition

0 to +5 Volts

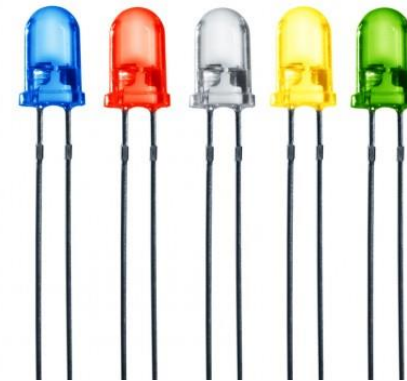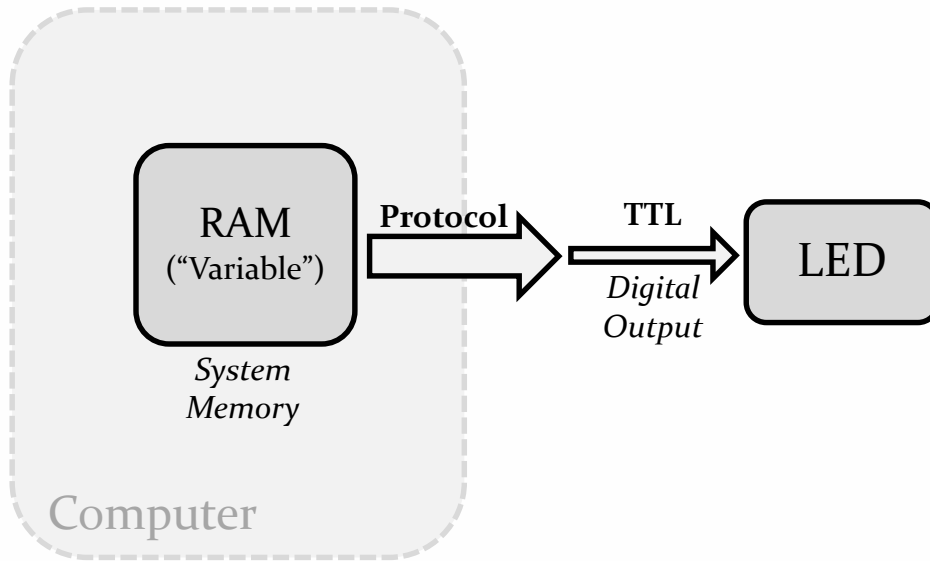


Utility



Digital Output

Conversely to acquisition, computers can only output voltages.

Definition

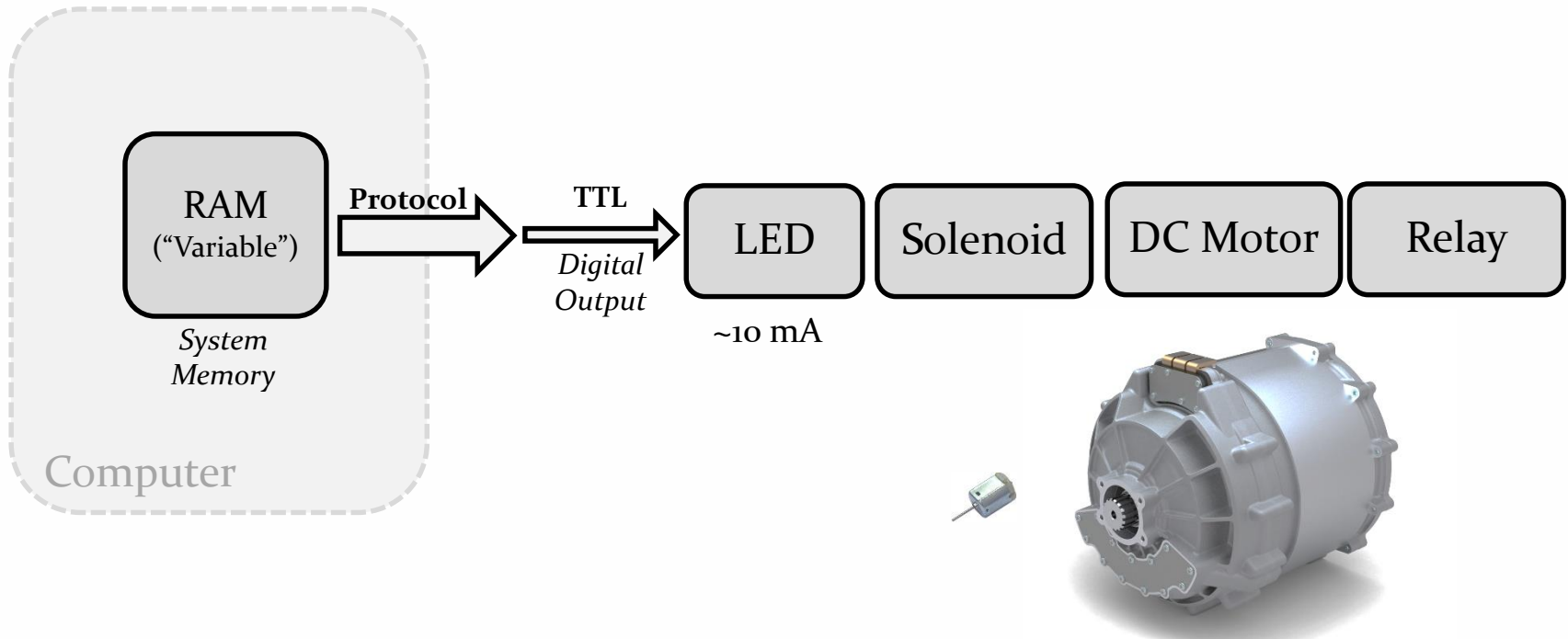

Can you start ("jump") your car with a USB port?


Utility



Electrical Load

An element in a circuit that consumes power. The more power consumed, the “heavier” the load.

Definition

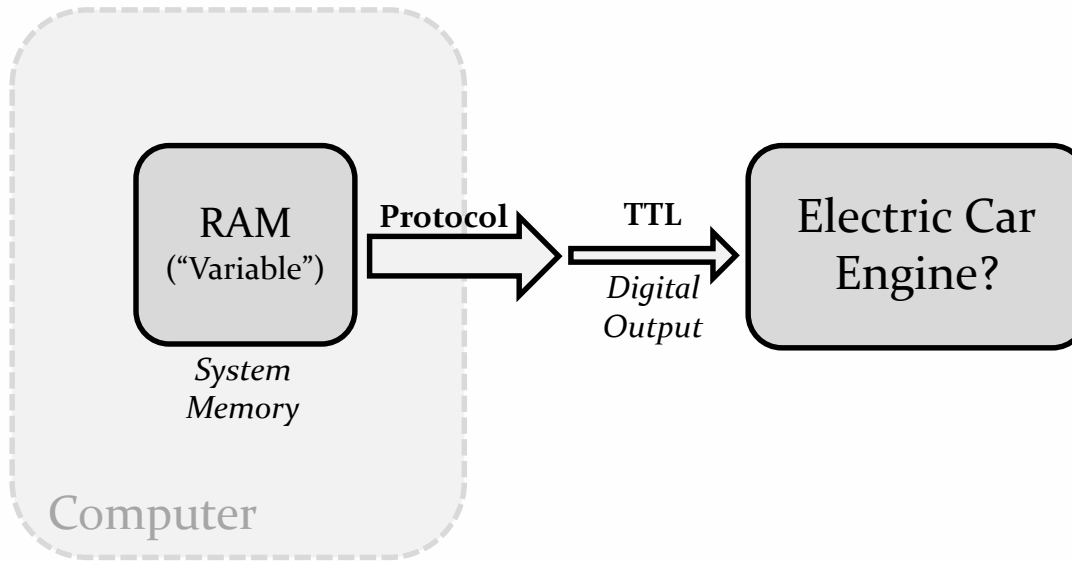

$$\text{Power} = V \cdot I = V \cdot R^2$$


Utility




Digital Output (Heavy Loads: $> 100 \text{ mA}$)

Conversely to acquisition, computers can only output voltages.

Definition

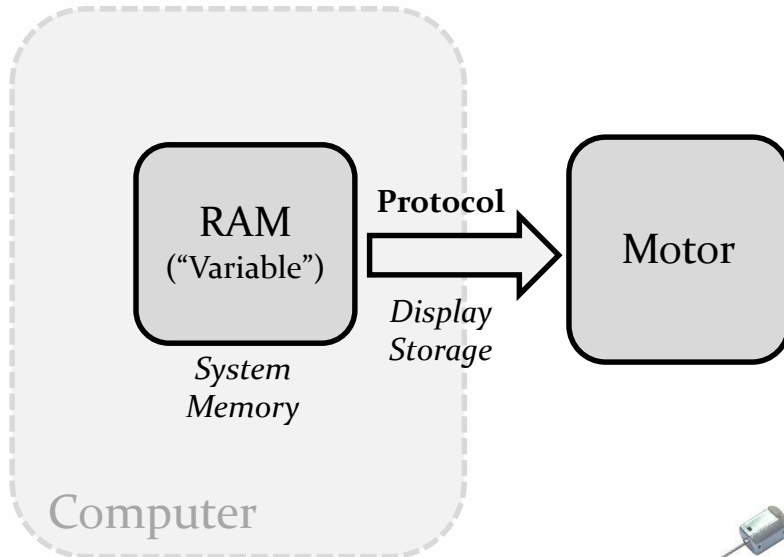

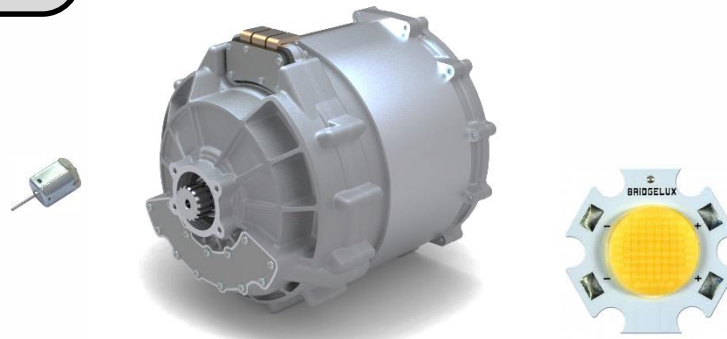- "Make something move"
- "Turn on the room lights"
- "Drive a high power laser"
- ...






Utility



Transistor (MOSFET) Switch

PN-Junction, Gate, Holes, Doping, and more!

Definition

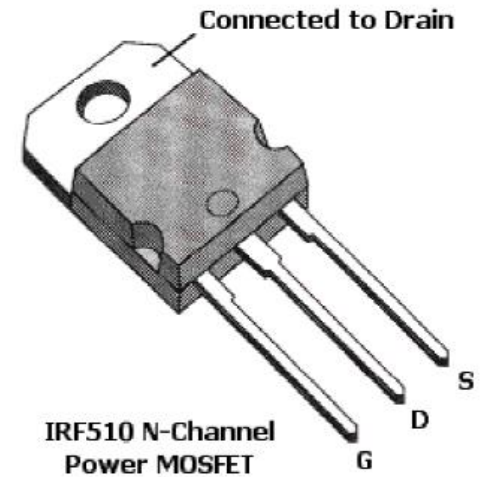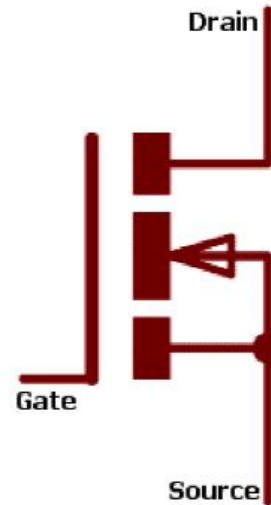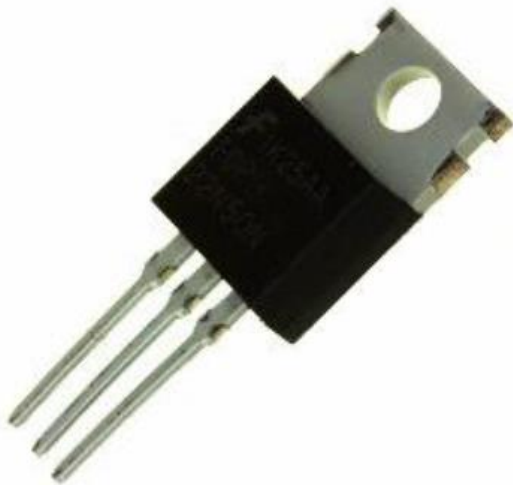

MOSEFT: Photo and Schematic of IRF510


Utility



The Silicon Transistor

PN-Junction, Gate, Holes, Doping, and more!

Definition

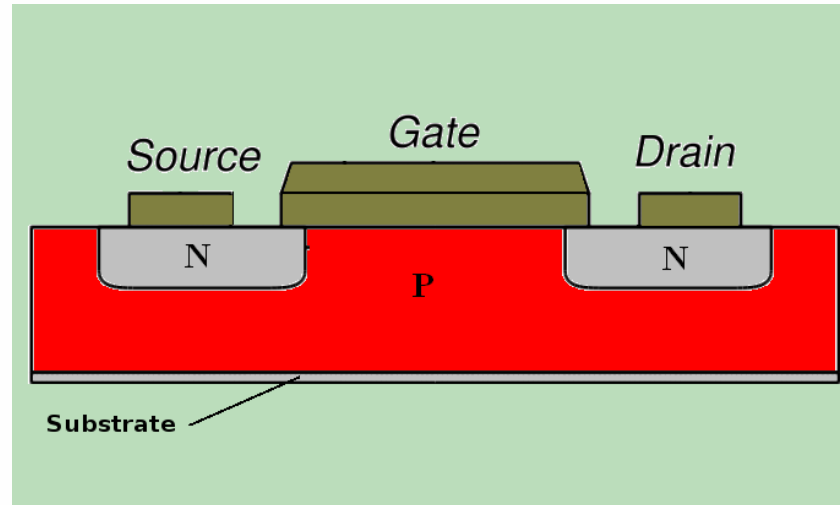

Utility





Transistor: Switching Inductive Loads

Current caused by induction can cause negative current flow (backwards), which can damage

Definition

Protection Diode

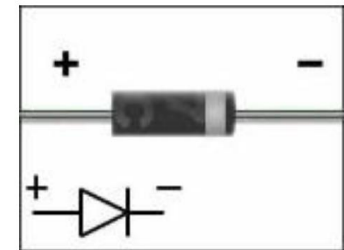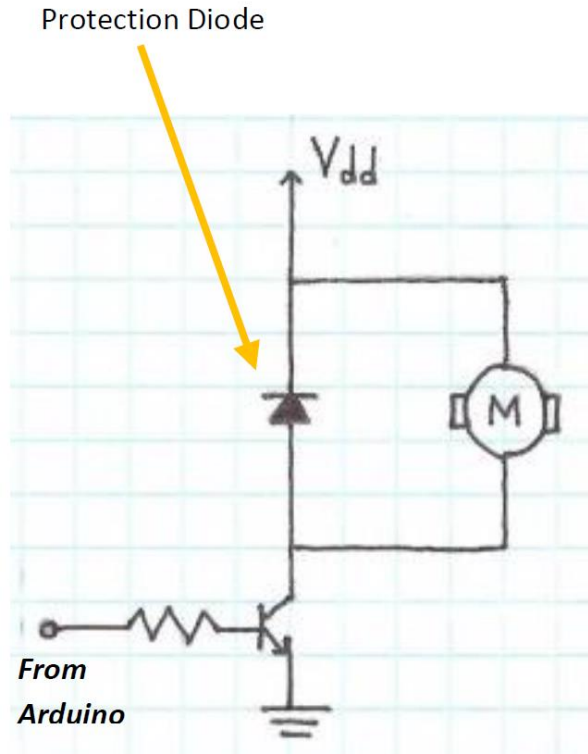

Diode: Picture and Schematic (with polarity)


Utility



Analog Output

Conversely to acquisition, computers can only output voltages.

Definition

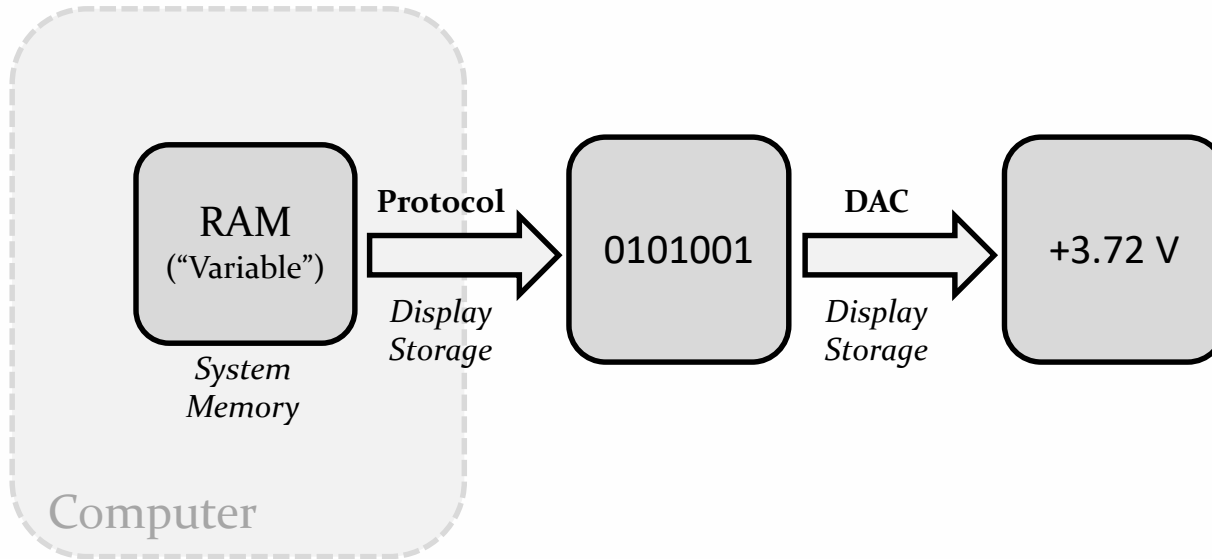


Utility



Digital-to-Analog Converter (DAC)


Conversely to acquisition, computers can only output voltages.

Definition

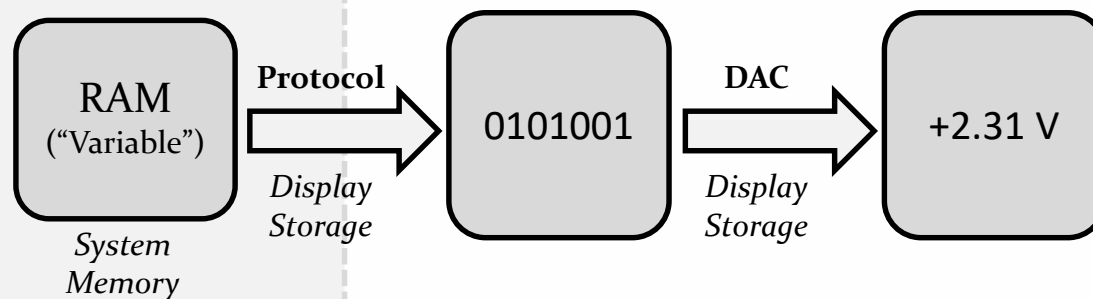

Computer

Note: The Arduino Uno has **no** DACs.

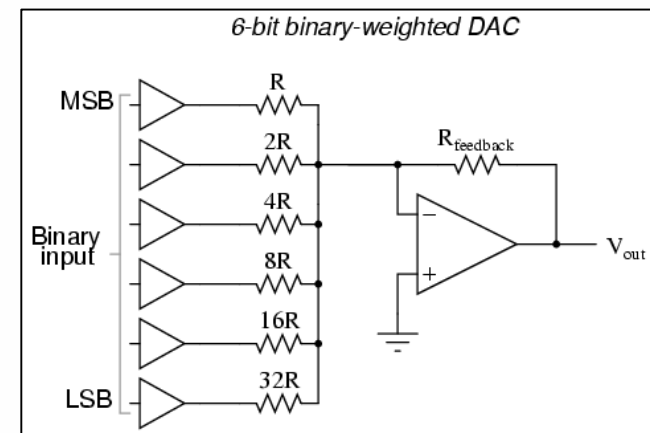


Utility



Pulse-Width Modulation (PWM)

Pesudo-Analog Output. Duty-cycle approximates an analog value.

Definition

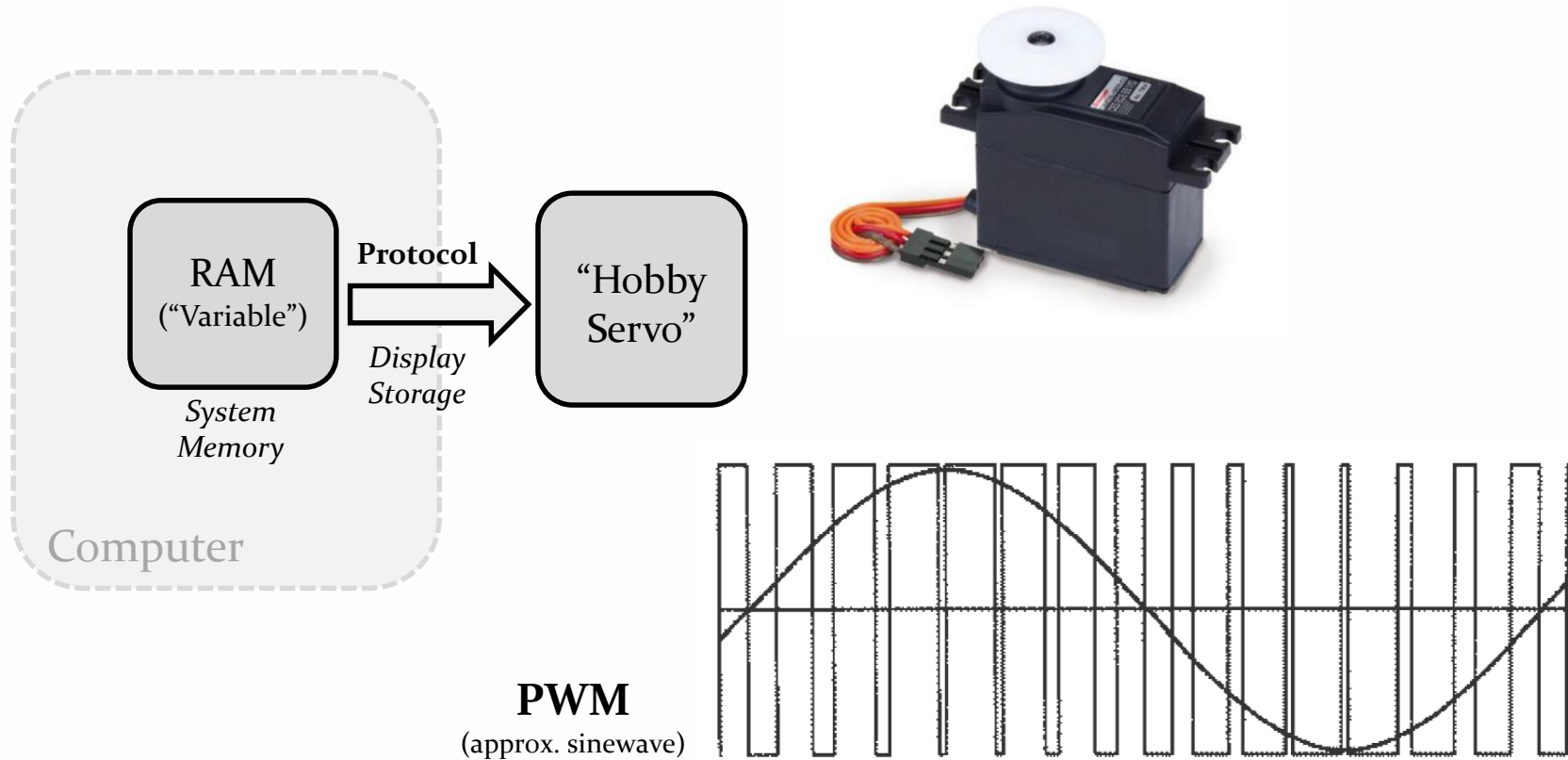


Utility



Vehicle Project

Autonomous Braitenberg vehicles that follow (or avoid) light.

Definition

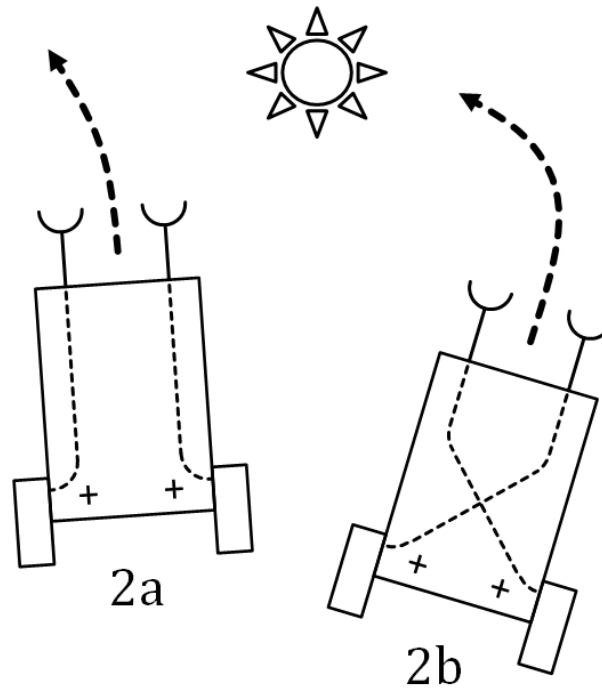

Utility